

PROBLEM #1


(a) Transfer function

$$V_- = V_+ = V_{in}$$

Node V_- :
$$\frac{V_{in} - V_{out}}{90k} + \frac{V_{in} - 0}{10k + \frac{1}{510^{-8}}} = 0$$

$$\frac{V_{out}}{V_{in}} = 1 + \frac{90k}{10k + \frac{1}{510^{-8}}} \leftarrow \text{could go directly to this using } 1 + \frac{Z_2}{Z_1}$$
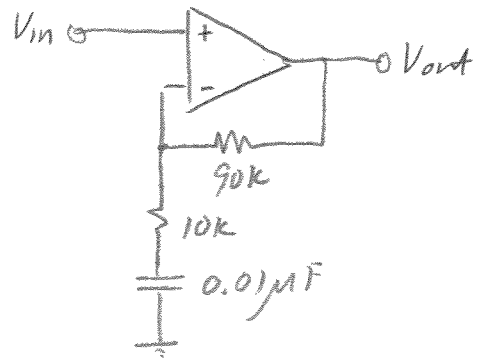
$$= \frac{10k + \frac{1}{510^{-8}} + 90k}{10k + \frac{1}{510^{-8}}} = \frac{510^{-3} + 1}{510^{-4} + 1} = \frac{10s + 10^3}{s + 10^4}$$



$$\frac{V_{out}}{V_{in}}(s) = \frac{10(s + 10^3)}{s + 10^4}$$

Bode Plots next page.

(b) Gain at DC: let $s \rightarrow 0$

$$\frac{V_{out}}{V_{in}} = \frac{10(0 + 10^3)}{0 + 10^4}$$

$$\frac{V_{out}}{V_{in}} = 1$$

(c) Impulse response

$$h(t) = \mathcal{L}^{-1} \left\{ \frac{10(s + 10^3)}{s + 10^4} \right\} = \mathcal{L}^{-1} \left\{ \frac{10(s + 10^4) - 9 \times 10^4}{s + 10^4} \right\} = \mathcal{L}^{-1} \left\{ 10 - \frac{9 \times 10^4}{s + 10^4} \right\}$$

$$h(t) = 10\delta(t) - 9 \times 10^4 e^{-10^4 t} u(t)$$

(d) Output if input is $2000t u(t)$.

$$V_{in}(s) = \frac{2000}{s^2} \quad V_{out}(s) = \frac{V_{out}(s)}{V_{in}(s)} V_{in}(s) = \frac{2 \times 10^4 (s + 10^3)}{s^2 (s + 10^4)}$$

$$V_{out}(s) = \frac{A}{s^2} + \frac{B}{s} + \frac{C}{s + 10^4}$$



$$A(s + 10^4) + Bs(s + 10^4) + Cs^2 = 2 \times 10^4 s + 2 \times 10^7$$

$$(B + C)s^2 + (A + 10^4 B)s + 10^4 A = 2 \times 10^7 \Rightarrow A = 2000, B = 1.8, C = -1.8$$

$$V_{out}(s) = \frac{2000}{s^2} + \frac{1.8}{s} - \frac{1.8}{s + 10^4}$$

$$V_{out}(t) = [2000t + 1.8 - 1.8e^{-10^4 t}] u(t)$$

PROBLEM #1 continued

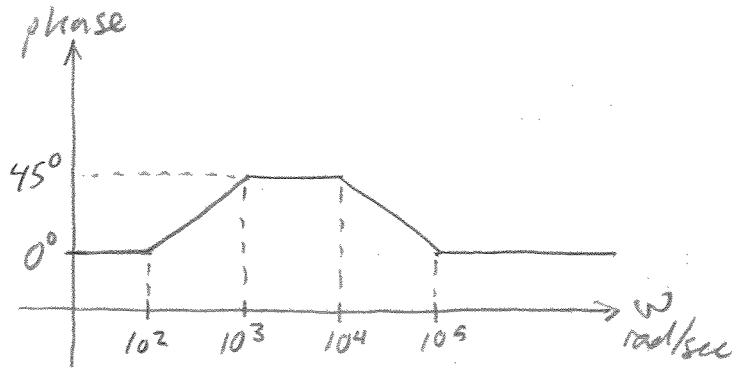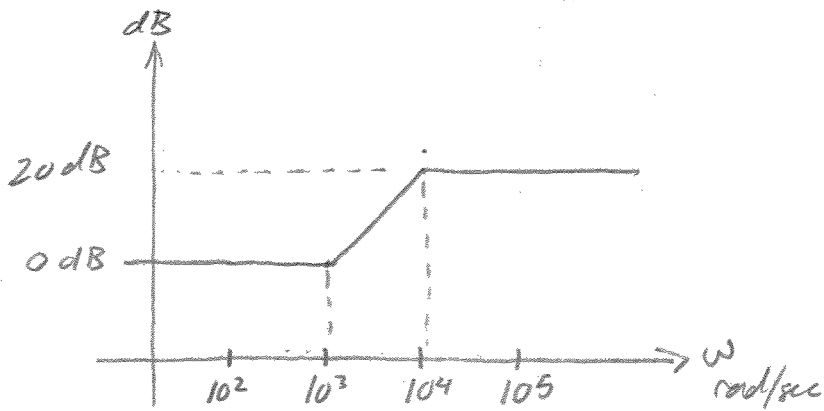

PROBLEM #2

(a) $GBW \approx A_0 \omega_0 = 5 \times 10^7 \text{ rad/sec} = 7.96 \text{ MHz} \approx 8 \text{ MHz}$

If $G=40$, $BW = \frac{8 \text{ MHz}}{40} = 200 \text{ kHz}$

(b) If $G=4$, $BW = \frac{8 \text{ MHz}}{4} = 2 \text{ MHz}$

(c) If $BW=100 \text{ kHz}$, $G = \frac{8 \text{ MHz}}{100 \text{ kHz}} = 80$



(d, e) Unity gain freq = $GBW = 8 \text{ MHz}$

PROBLEM #3

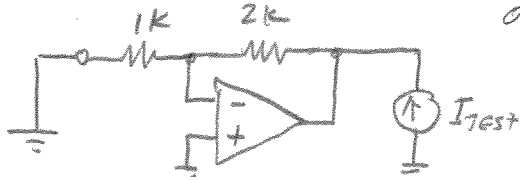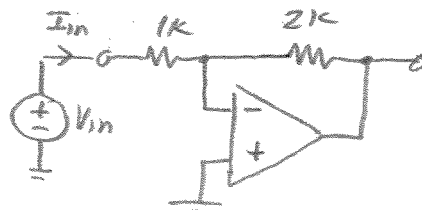(a) Ideal Case

$$G = -\frac{R_2}{R_1} = -\frac{2k}{1k} \Rightarrow \boxed{G = -2}$$

$$I_{in} = \frac{V_{in} - V_-}{1k} = \frac{V_{in} - 0}{1k} \quad R_{in} = \frac{V_{in}}{I_{in}} \Rightarrow \boxed{R_{in} = 1k\Omega}$$




output impedance

$$V_- = 0 \text{ so: } \frac{0-0}{1k} + \frac{0-V_{out}}{2k} = 0 \Rightarrow V_{out} = 0$$

$$R_{out} = \frac{V_{out}}{I_{test}} \Rightarrow \boxed{R_{out} = 0}$$

(b)

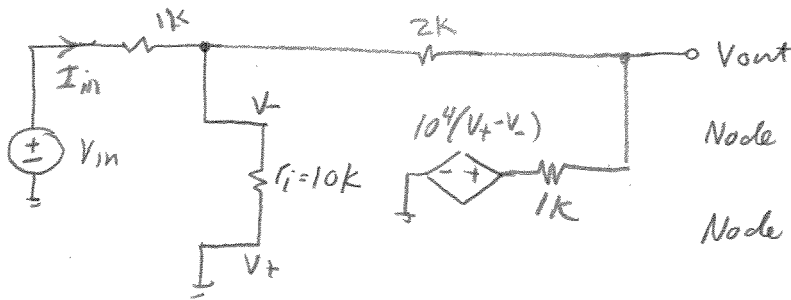

$$\text{Node } V_-: \frac{V_- - V_{in}}{1k} + \frac{V_- - 0}{10k} + \frac{V_- - V_{out}}{2k} = 0$$

$$\text{Node } V_{out}: \frac{V_{out} - V_-}{2k} + \frac{V_{out} - 10^4(0 - V_-)}{1k} = 0$$

Simplify first eqn: $V_- \left(\frac{1}{1k} + \frac{1}{10k} + \frac{1}{2k} \right) = \frac{V_{in}}{1k} + \frac{V_{out}}{2k}$

$$\Rightarrow V_- (10 + 1 + 5) = 10V_{in} + 5V_{out} \Rightarrow V_- = \frac{10}{16}V_{in} + \frac{5}{16}V_{out}$$

Substitute into 2nd:

$$\frac{V_{out} - \left(\frac{10}{16}V_{in} + \frac{5}{16}V_{out} \right)}{2k} + \frac{V_{out} - 10^4 \left(\frac{10}{16}V_{in} + \frac{5}{16}V_{out} \right)}{1k} = 0$$

$$V_{out} \left(\frac{1}{2k} - \frac{5}{16(2k)} + \frac{1}{1k} - \frac{10^4(5)}{16(1k)} \right) = V_{in} \left(\frac{10}{16(2k)} + \frac{10^4(10)}{16(1k)} \right)$$

$$V_{out} (-3.12565625) = V_{in} (6.2503125) \Rightarrow \boxed{\frac{V_{out}}{V_{in}} = -1.99968}$$

(c) Input resistance: Use same circuit


$$I_{in} = \frac{V_{in} - V_-}{1k} = \frac{V_{in} - \left(\frac{10}{16}V_{in} + \frac{5}{16}V_{out} \right)}{1k} = \frac{V_{in} - \left(\frac{10}{16}V_{in} + \frac{5}{16}(-1.99968)V_{in} \right)}{1k}$$

$$I_{in} = \frac{0.9999}{1k} V_{in} \quad R_{in} = \frac{V_{in}}{I_{in}} = \frac{1k}{0.9999} \quad \boxed{R_{in} = 1.0001k\Omega}$$

(You could let $V_{in} = 1V$ if you wanted - same answer)

PROBLEM #3 continued

(d) Output resistance

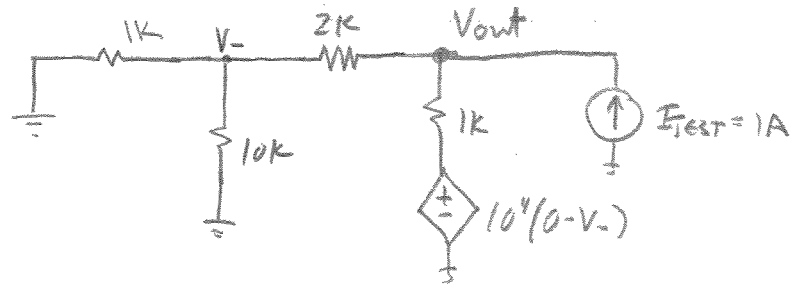

$$\frac{V_- - 0}{1k} + \frac{V_- - 0}{10k} + \frac{V_- - V_{out}}{2k} = 0.$$

$$\frac{V_{out} - V_-}{2k} + \frac{V_{out} + 10^4 V_-}{1k} - 1 = 0.$$

From first equation $V_- = 0.3125 V_{out}$. Substitute into 2nd equation

$$\frac{V_{out} - 0.3125 V_{out}}{2k} + \frac{V_{out} + 10^4 (0.3125 V_{out})}{1k} = 1 \Rightarrow V_{out} = 0.3199$$



$$R_{out} = \frac{V_{out}}{I_{TEST}} \Rightarrow R_{out} = 0.3199 \Omega$$

PROBLEM #4

Unity gain frequency = 3 MHz = 1.88 Mrad/sec. = ω_{0dB}

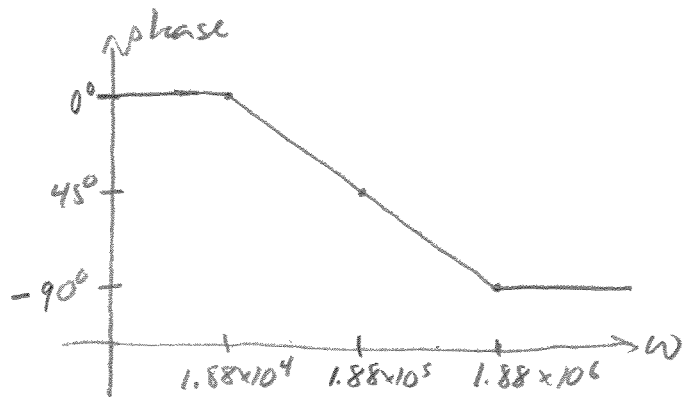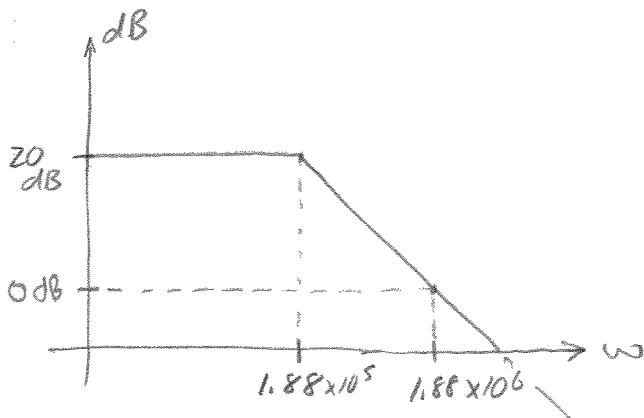(a) $H(s) \approx \frac{\omega_{0dB}}{s + \frac{\omega_{0dB}}{G}}$ where G is ideal DC gain.

$$H(s) = \frac{1.88 \times 10^6}{s + 1.88 \times 10^5}$$




(b) Step response: $V_{in}(t) = u(t)$ $V_{in}(s) = \frac{1}{s}$.

$$V_{out}(s) = \frac{V_{out}}{V_{in}}(s) V_{in}(s) = N(s) V_{in}(s) = \frac{1.88 \times 10^6}{s(s + 1.88 \times 10^5)} = \frac{A}{s} + \frac{B}{s + 1.88 \times 10^5}$$

$$A = 10, B = -10. \Rightarrow V_{out}(s) = \frac{10}{s} - \frac{10}{s + 1.88 \times 10^5}$$
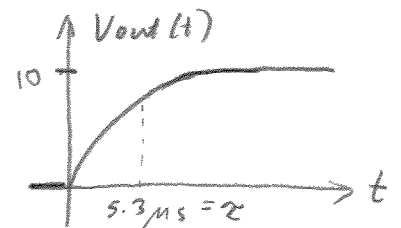
$$V_{out}(t) = (10 - 10e^{-1.88 \times 10^5 t}) u(t)$$



PROBLEM #4 continued

(c) Sinusoidal steady state $s = j\omega$, use phasor analysis

$$V_{in}(t) = 3\cos(4 \times 10^6 t) \Rightarrow V_{in} = 3\angle 0^\circ, \quad s = j\omega = j4 \times 10^6$$

$$\frac{V_{out}}{V_{in}} = \frac{1.88 \times 10^6}{j4 \times 10^6 + 1.88 \times 10^5} = 0.4695\angle -87.3^\circ$$

$$V_{out} = \frac{V_{out}}{V_{in}} V_{in} = (0.4695\angle -87.3^\circ)(3\angle 0^\circ) = 1.408\angle -87.3^\circ$$

$$V_{out}(t) = 1.408 \cos(4 \times 10^6 t - 87.3^\circ) \text{ Volts}$$

PROBLEM #5

Node V_+ : $\frac{V_+ - V_1}{1k} + \frac{V_+ - 0}{10k} = 0$

$$\Rightarrow V_+ = V_1 \frac{10}{11}$$

Node V_- : $\frac{V_- - V_2}{1k} + \frac{V_- - A(V_+ - V_-)}{10k} = 0$

substitute for V_+ : $\frac{V_- - V_2}{1k} + \frac{V_- - A\left(\frac{10}{11}V_1 - V_-\right)}{10k} = 0$

$$V_- \left(\frac{1}{1k} + \frac{1}{10k} + \frac{A}{10k} \right) = \frac{A\left(\frac{10}{11}\right)V_1}{10k} + \frac{V_2}{1k} \Rightarrow V_- (A+11) = A\frac{10}{11}V_1 + 10V_2$$

$$V_- = \frac{A\left(\frac{10}{11}\right)V_1 + 10V_2}{A+11} = \frac{10AV_1 + 110V_2}{11A+121}$$

Then $V_{out} = A(V_+ - V_-)$


$$V_{out} = A \left(V_1 \frac{10}{11} - \frac{10AV_1 + 110V_2}{11A+121} \right) = A \frac{V_1(10)(A+11) - (10AV_1 + 110V_2)}{11A+121}$$

$$= A \frac{110(V_1 - V_2)}{11A+121} \Rightarrow \frac{V_{out}}{V_{in}} = \frac{10A(V_1 - V_2)}{A+11}$$


(b) $\lim_{A \rightarrow \infty} \frac{V_{out}}{V_{in}} = 10(V_1 - V_2)$

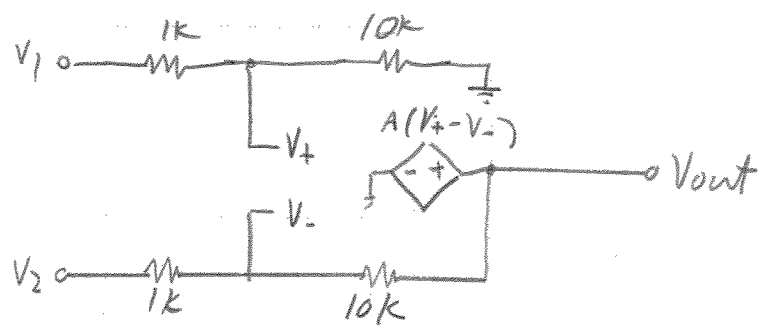(c) If $V_1 = 1V, V_2 = 0V$, Ideal Value is $10V$. 1% diff = 9.9 Volts.

$$9.9 = \frac{10A(1-0)}{A+11} \quad \Rightarrow \quad A \geq 1089$$



PROBLEM #6

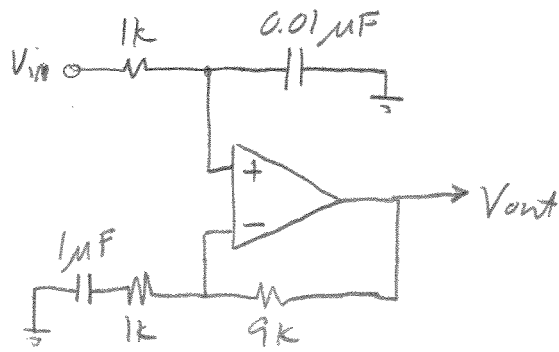

$$(b) \frac{V_+ - V_{in}}{1k} + \frac{V_+ - 0}{1/s10^{-8}} = 0 \quad (\text{Node } V_+)$$

or use voltage divider.


$$V_+ = V_{in} \frac{1/s10^{-8}}{1/s10^{-8} + 1k} = V_{in} \frac{10^5}{s + 10^5}$$

$$\text{Node } V_-: \frac{V_- - 0}{1k + \frac{1}{s10^{-6}}} + \frac{V_- - V_{out}}{9k} = 0 \Rightarrow V_{out} = V_- \frac{1k + \frac{1}{s10^{-6}} + 9k}{1k + \frac{1}{s10^{-6}}}$$

$$V_{out} = V_- \frac{s10^{-2} + 1}{s10^{-3} + 1} = V_- \frac{10s + 1000}{s + 1000} = \frac{10(s + 100)}{(s + 1000)} V_-$$

$$\text{Then use } V_- = V_+ = V_{in} \frac{10^5}{s + 10^5}$$
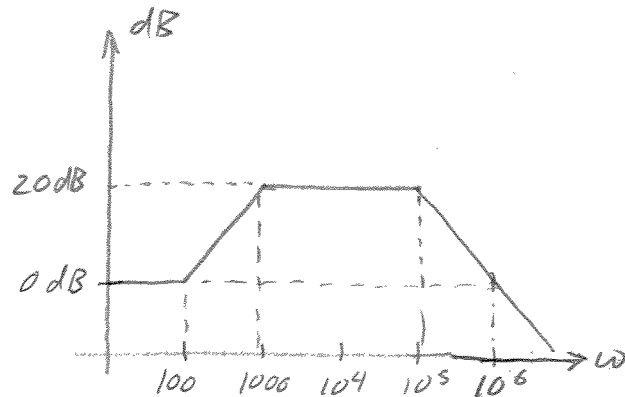
$$\frac{V_{out}}{V_{in}} = \frac{10^6 (s + 100)}{(s + 1000)(s + 10^5)}$$



(a) Let $s \rightarrow 0$.

$$\frac{V_{out}}{V_{in}} = \frac{10^6 (100)}{(1000)(10^5)} = 1$$

(d) If $V_{in} = 2u(t)$, $V_{in}(s) = \frac{2}{s}$

$$V_{out}(s) = \frac{V_{out}}{V_{in}}(s) V_{in}(s) = \frac{2 \times 10^6 (s + 100)}{s(s + 1000)(s + 10^5)}$$

$$V_{out}(s) = \frac{A}{s} + \frac{B}{s + 1000} + \frac{C}{s + 10^5} \rightarrow A = 2, B = 18.18, C = -20.1818$$

$$V_{out}(s) = \frac{2}{s} + \frac{18.18}{s + 1000} - \frac{20.18}{s + 10^5}$$

$$V_{out}(t) = [2 + 18.18e^{-10^3 t} - 20.18e^{-10^5 t}] u(t)$$